

Surveillance Robot - Complete Connection Sheet

Arduino Uno ↔ L298N Motor Driver		
L298N	Arduino Uno	
IN1	D2	
IN2	D3	
IN3	D4	
IN4	D7	
ENA	Jumper ON	
ENB	Jumper ON	
GND	GND	

Arduino Uno ↔ Ultrasonic Sensor (HC-SR04)

HC-SR04	Arduino Uno
VCC	5V
GND	GND
TRIG	D9
ECHO	D10

Arduino Uno ↔ Scanner Servo (Ultrasonic Rotation)

Servo Wire	Arduino Uno
Signal	D5
VCC	5V
GND	GND

Arduino Uno ↔ Laser Module

Laser module	Arduino Uno
+	D8
-	GND

Motor Connections

Left Side Motors (Parallel)

motor	L298N
Left front motor+	OUT1
Left front motor-	OUT2

Left Rear motor+	OUT1
Left Rear motor-	OUT2

Right Side Motors (Parallel)

Motor	L298N
Right Front Motor+	OUT3
Right Front Motor-	OUT4
Right Rear Motor+	OUT3
Right Rear Motor-	OUT4

Battery Connections

Motor Battery

Battery	L298N
+	12V/VIN
-	GND